

# Lab 0 introduction

---

## Index

[Sequential Circuit Introduction](#)

[Coding Style](#)

[\*\*Naming conventions\*\*](#)

[\*\*Reg/Wire declaration\*\*](#)

[\*\*Coding Precautions\*\*](#)

[\*\*Latch\*\*](#)


[\*\*Reset\*\*](#)

[FSM](#)

[REFERENCE](#)

# The difference between Combinational circuit and Sequential circuit

## Combinational Circuit

 

- Take some combinational logic circuits for example. Logic gate(e.g. and, or...), MUX, Decoder, Selector...
- Coding example:

```
//assign
wire a,b,c;
assign a = b & c;

//always block
reg a; // this is not a DFF
wire b,c;
always @(*) begin
    a = b & c;
end
```

## Sequential Circuit

 


Figure: Sequential Circuit

- Sequential elements are used for storage
- Coding example:

```
//synchronous negedge reset
reg a; // this is a DFF
wire b;
always @(posedge clk) begin
    if(!rst_n) a <= 0;
    else a <= b;
end

//asynchronous posedge reset
reg a; // this is a DFF
wire b;
always @(posedge clk or posedge rst) begin
    if(rst) a <= 0;
    else a <= b;
end
```

# Coding Style

## Naming conventions

- rst for reset, clk for clock
- \_n for active-low
- Using \_ rather than - in naming reg/wire
- Naming must be meaningful
- Naming example: I want to define a flag that represents reg A larger than reg B, it can call A\_lr\_B or A\_larger\_B.
- uppercase letters and lowercase letters are different in Verilog.
- You can use uppercase letters or \_ to separate reg/wire naming variables. For example, current\_state or currentState.
- Use uppercase letters for names of constants and user-defined types.  
e.g. `define BUS\_LENGTH 32 or localparam BUS\_LENGTH = 32
- Use lowercase letters for all signals, variables, and ports.  
e.g. wire clk, rst...
- Other naming conventions
  - \*\_r: register type(DFF)
  - \*\_w: wire type or reg type but represent combinational logic.

## Reg/Wire declaration

- Using little-endian for vector initialization, for example, reg [7:0] counter or wire [7:0] adderResult.
- Using big-endian for multi-bit array declaration, for example, reg [31:0] mem [0:31].

## Coding Precautions

- Adding some proper comments or documentation for recording.
- Avoid using both edges of a clock due to the reason that it is difficult for DFT(Design-For Testability) process.
- Avoid tri-state buses
- Codes must be synthesizable. For example  
assign, always block, called sub-modules, if-else if-else, cases, parameter, operators
- *Bitwise operators* — perform operations on each bit of a vector  
~ & | ^ ^~ ~^
- *Unary reduction operators* — collapse a vector to a 1-bit result  
~ & | ^ ~& ~| ^~ ~^
- *Logical operators* — return a true/false result, based on a logical test  
&& ||
- *Equality, relational operators* — return true/false, based on a comparison  
= = != < <= > >=
- *Shift operators* — shift the bits of a vector left or right  
<< <<< >> >>>
- *Concatenate operators* — join multiple expressions into a vector  
{ } {n{ }}
- *Conditional operator* — selects one expression or another  
?:
- *Arithmetic operators* — perform integer and floating point math  
+ - \* / % \*\*
- Data has to be described in one always block, for example

```
//multiple source drive is not allow
always @(posedge clk) begin
    if(!rst_n) out_r <= 'd0;
    else out_r <= out_r + 'd1;
end
always @(posedge clk) begin
    if(ready) out_r <= 'd1;
end

//correct
always @(posedge clk) begin
    if(!rst_n) out_r <= 'd0;
    else if(ready) out_r <= 'd1;
    else out_r <= out_r + 'd1;
end
```

- Only use "<=" when you are writing sequential blocks, and do not use "<=" and "=" in one always block.
- Avoid assigning unknown or high impedance values in your code.

- Bit width must be matching when you are using an assigned statement. For example

```
wire [3:0] a;  
wire [2:0] b;  
assign a = b // this is not allowed
```

- Avoid combination feedback circuits, for example

```
//wire feedback is not allowed  
wire [1:0] a = a + 'd1;  
  
//correct  
reg [1:0] a_r;  
wire [1:0] a = a_r + 'd1;  
always @(posedge clk) begin  
    if(!rst_n) a_r <= 'd0;  
    else a_r <= a;  
end
```

- Suggest using only a variable in one always block.

```
reg [1:0] a_r,b_r;  
// bad  
always @(posedge clk) begin  
    if(!rst_n) begin  
        a_r <= 'd0;  
        b_r <= 'd0;  
    end  
    else if(trigger_1) b_r <= 'd1;  
    else a_r <= 'd2;  
end  
  
// good  
always @(posedge clk) begin  
    if(!rst_n) begin  
        a_r <= 'd0;  
    end  
    else a_r <= 'd2;  
end  
always @(posedge clk) begin  
    if(!rst_n) begin  
        b_r <= 'd0;  
    end  
    else if(trigger_1) b_r <= 'd1;  
end
```

- Suggest combinational and sequential logic separating.

```
// bad
always @(posedge clk or negedge rst_n) begin
    if(!rst_n) begin
        cur_state <= IDLE;
    end
    else begin
        if (cal_start) cur_state <= CAL;
        else if(cal_done) cur_state <= OUT
        else if(out_done) cur_state <= IDLE;
    end
end

//good
always @(posedge clk or negedge rst_n) begin
    if(!rst_n) begin
        cur_state <= IDLE;
    end
    else begin
        cur_state <= next_state;
    end
end
always @(*) begin
    case(curr_state)
        IDLE : next_state = cal_start ? CAL : IDLE;
        CAD : next_state = cal_done ? OUT : CAD;
        OUT : next_state = out_done ? IDLE : OUT;
        default : next_state = IDLE;
    end
```

## Latch

- Avoid using Latch in your code. For example
  1. Using case statements without default declaration in combination circuit.
  2. Using if-else if-else statement without else in combination circuit.

```
// case 1 : lack of else
always @(*) begin
    if(m==2'd0) out_w = 2'd0;
    else if(m==2'd1) out_w = 2'd1;
end

// case 2 : lack of default
always @(*) begin
    case(m)
        2'd0: out_w = 2'd0;
        2'd1: out_w = 2'd1;
    end

// case 1 : correct
always @(*) begin
    if(m==2'd0) out_w = 2'd0;
    else if(m==2'd1) out_w = 2'd1;
    else out_w = 2'd2;
end

// case 2 : correct
always @(*) begin
    case(m)
        2'd0: out_w = 2'd0;
        2'd1: out_w = 2'd1;
        default: out_w = 2'd2;
    end
```

## Reset

- Remember to reset all storage elements

This can help you avoid accepting unknown signals.




- Some Poor coding style example

```
//poor example
always @(posedge clk) begin
    if(!rst_n || !a) sig_r <= 'd0;
    else sig_r <= a;
end

//suggest example
always @(posedge clk) begin
    if(!rst_n) sig_r <= 'd0;
    else if(!a) sig_r <= 'd0';
    else sig_r <= a;
end
```

## FSM

- Mealy\_vs\_Moore

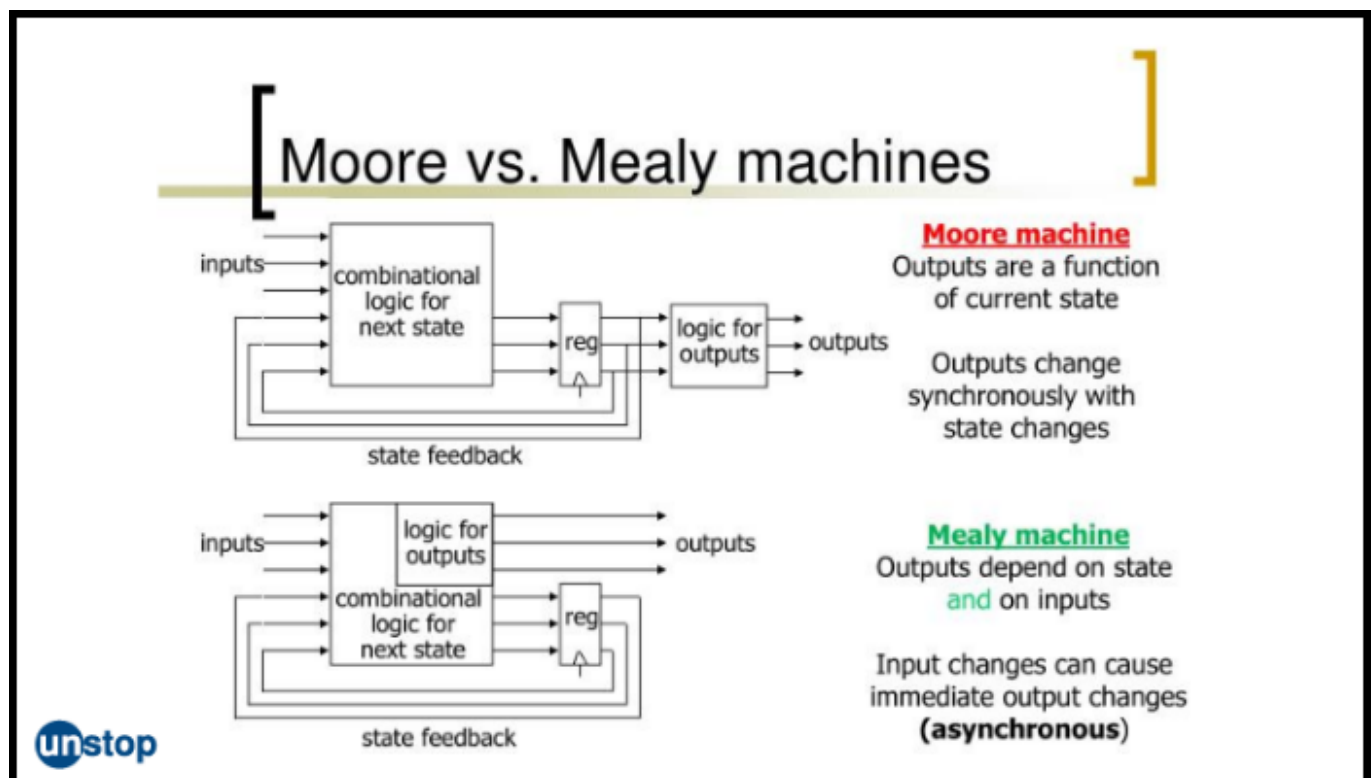

Coding Example:

```
//current state logic
always @(posedge d_clk or negedge rst_n) begin
    if(!rst_n) begin
        curr_state <= IDLE;
    end
    else begin
        curr_state <= next_state;
    end
end
```

```

        end
    end
    //mealy machine next state logic
    always @(curr_state or input_value) begin
        case (curr_state)
            IDLE : next_state = input_value[0] ? CAL : IDLE;
            CAL  : next_state = input_value[1] ? ...;
            DONE : next_state = DONE;
            default : ...;
        endcase
    end
    //Moore machine next state logic
    always @(curr_state) begin
        case (curr_state)
            IDLE : next_state = trigger_1 ? CAL : IDLE;
            CAL  : next_state = trigger_2 ? ...;
            DONE : next_state = DONE;
            default : ...;
        endcase
    end
end

```

## Introduce 3 level circuit

- [Behavioral level](#)
- [Dataflow level](#)
- [Gate level or Structural level](#)

### Behavioral level

#### 1. initial block

- Usually used for writing testbench.
- non synthesizable

#### 2. always block

- Used for reg type variable
- Describing sequential circuit or combinational circuit.

### Dataflow level


```

wire [1:0] a;
wire b,c;
//case 1
assign a = {b,c}; //concatenate
//case 2
assign a = {b,1'b0}; //concatenate
//case 3
assign a = {2{1'b0}}; //concatenate

```
 
## Gate level or Structural level

```
module comparator( A, B, gt, lt, eq );  
    input A, B;  
    output gt, lt, eq;  
  
    wire negA, negB;  
  
    not not1( negA, A );  
    not not2( negB, B );  
    and and1( gt, A, negB );  
    and and2( lt, negA, B );  
    xnor xnor1( eq, A, B );  
  
endmodule
```



## REFERENCE

1. Combinational circuit

<https://www.javatpoint.com/combinational-logic-circuits-in-digital-electronics>

2. sequential Circuit

<https://www.geeksforgeeks.org/introduction-of-sequential-circuits/>

3. Mealy vs Moore

<https://unstop.com/blog/difference-between-mealy-and-moore-machine>

4. 描述電路的三種層次 - HackMD

[https://hackmd.io/@dppa1008/BJWS5\\_B\\_G?type=view](https://hackmd.io/@dppa1008/BJWS5_B_G?type=view)

5. Verilog Synthesis Methodology

[https://people.ece.cornell.edu/land/courses/ece5760/Verilog/coding\\_and\\_synthesis\\_with\\_verilog.pdf](https://people.ece.cornell.edu/land/courses/ece5760/Verilog/coding_and_synthesis_with_verilog.pdf)