

# Improving Timing, Area, and Power

<Ref> Verilog Styles for Synthesis of Digital Systems, Smith/Franzon, Prentice-Hall 2000

- Timing Issues in Design
- Low-Power Issues in Design
- Area Issues in Design

# Timing Issues in Design



**Performance** and **Implementation area** are fundamental importance in the design of a digital system.



Timing-related design issues have a big influence on both of these.


Performance measure is

- **Latency** : How long does it take to complete a particular operation ?
- **Throughput** : How many operations can be completed per second ?


- In general, the **throughput** of an ASIC is defined as a function of two factors:

$$\textit{Throughput} = f_{\textit{clock}} / \textit{CPO}$$

Where

 

 $f_{\textit{clock}}$  is the clock frequency .




CPO is the cycles per operation.

- how many clock ticks transpire between the completion of each operation.
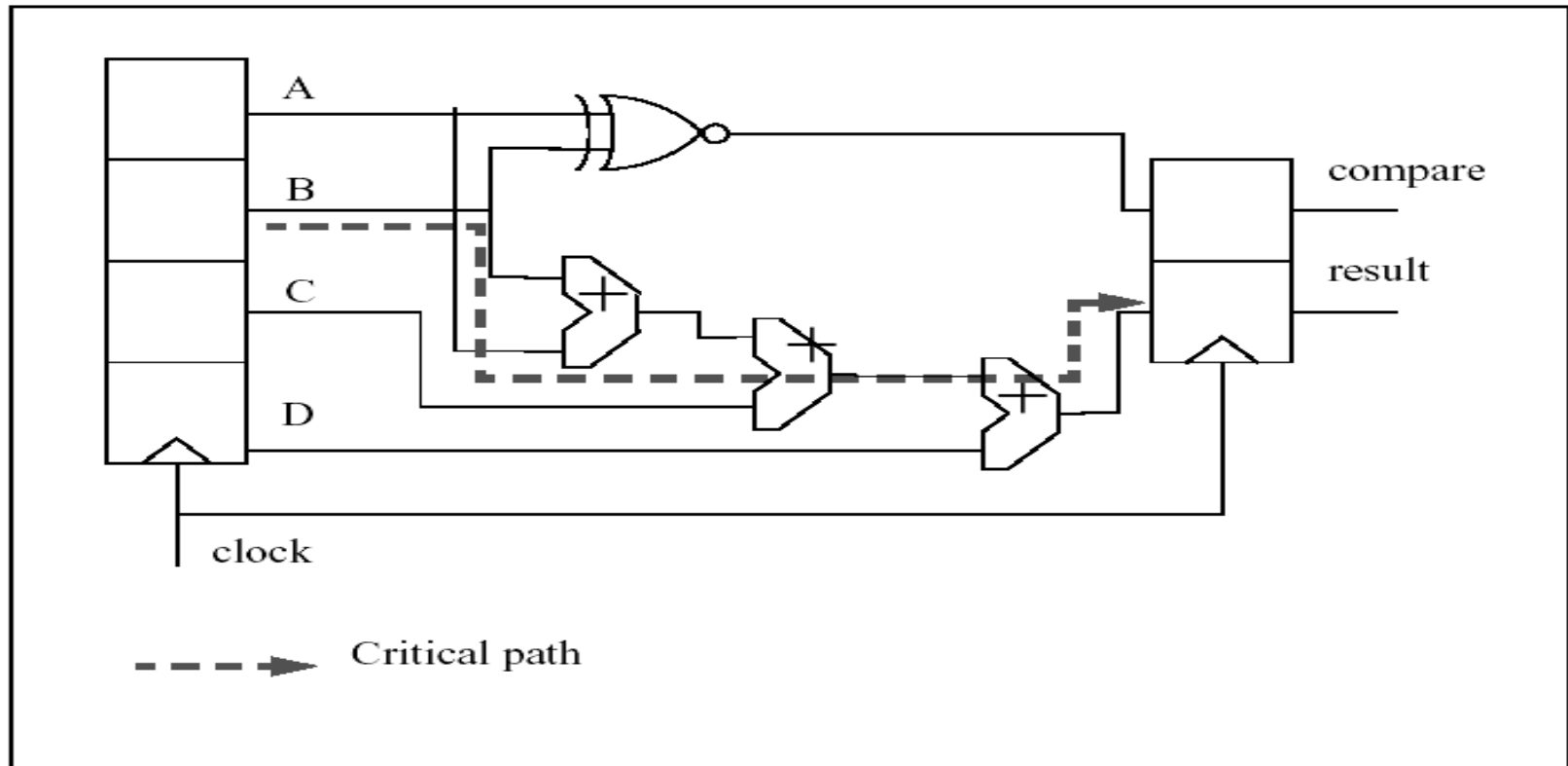
## Original specification fragment and corresponding critical path


```
always@(posedge clock)
begin
  result <= A + B + C + D;
  compare <= A ^ B;
end
```




## Modified specification fragment & corresponding critical path.

```
always @(posedge clock)
begin
    interimResult1 <= A + B;
    Cnew <= C;
    Dint <= D;
    Dnew <= Dint;
    interimResult2 <= InterimResult1 + Cnew;
    Result <= InterimResult2 + Dnew;
    InterimCompare1 <= A^B;
    InterimCompare2 <= InterimCompare1;
    Compare <= InterimCompare2;
end
```

# Pipelined Design

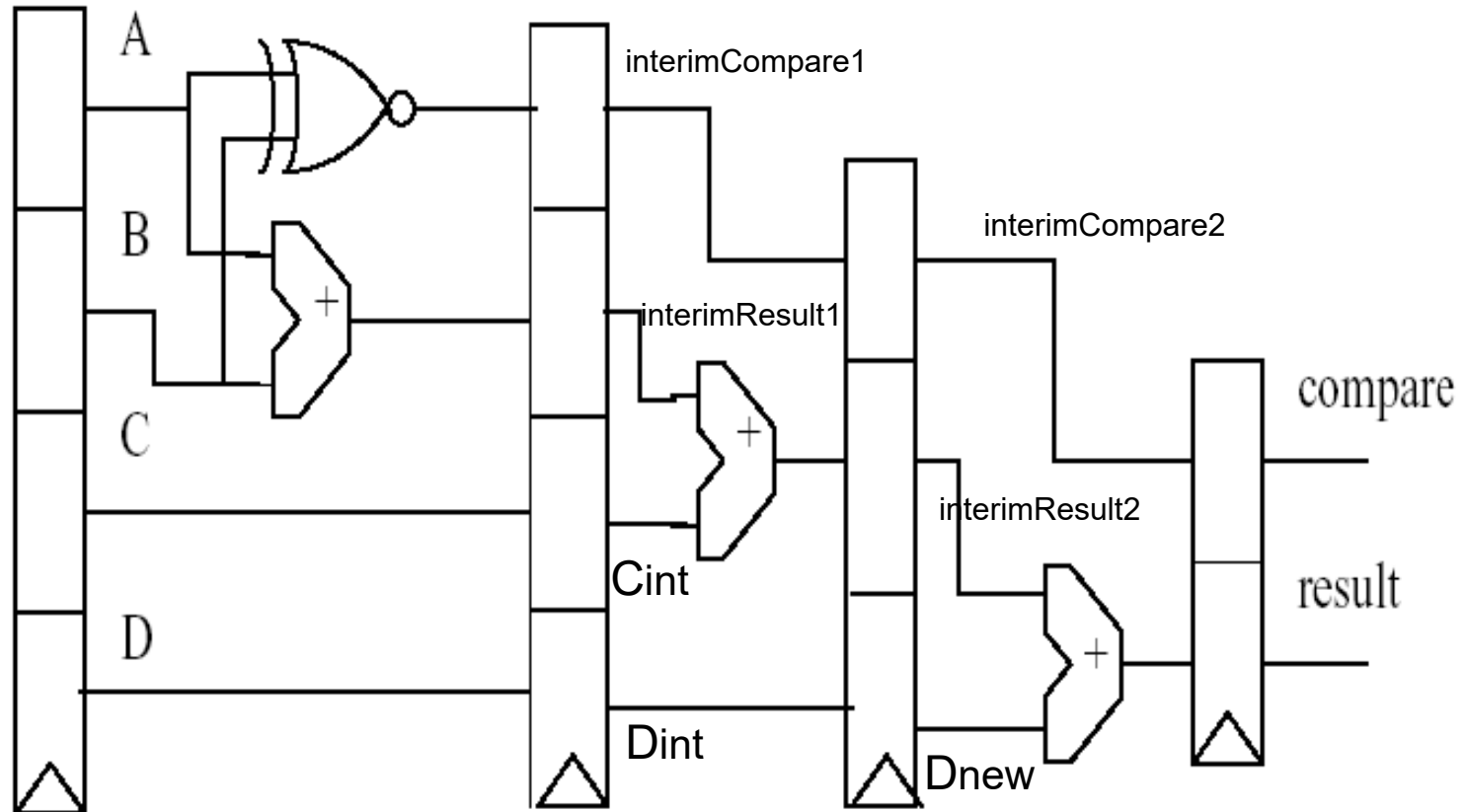


## Typical Clock Distribution Scheme

 

- The delay calculators are used by timing analysis tools, during and after synthesis.
- The clock tree is designed to attempt to ensure that the delay from the clock source to each of the clock leaves is identical.




# Basic Flip-flop Operation

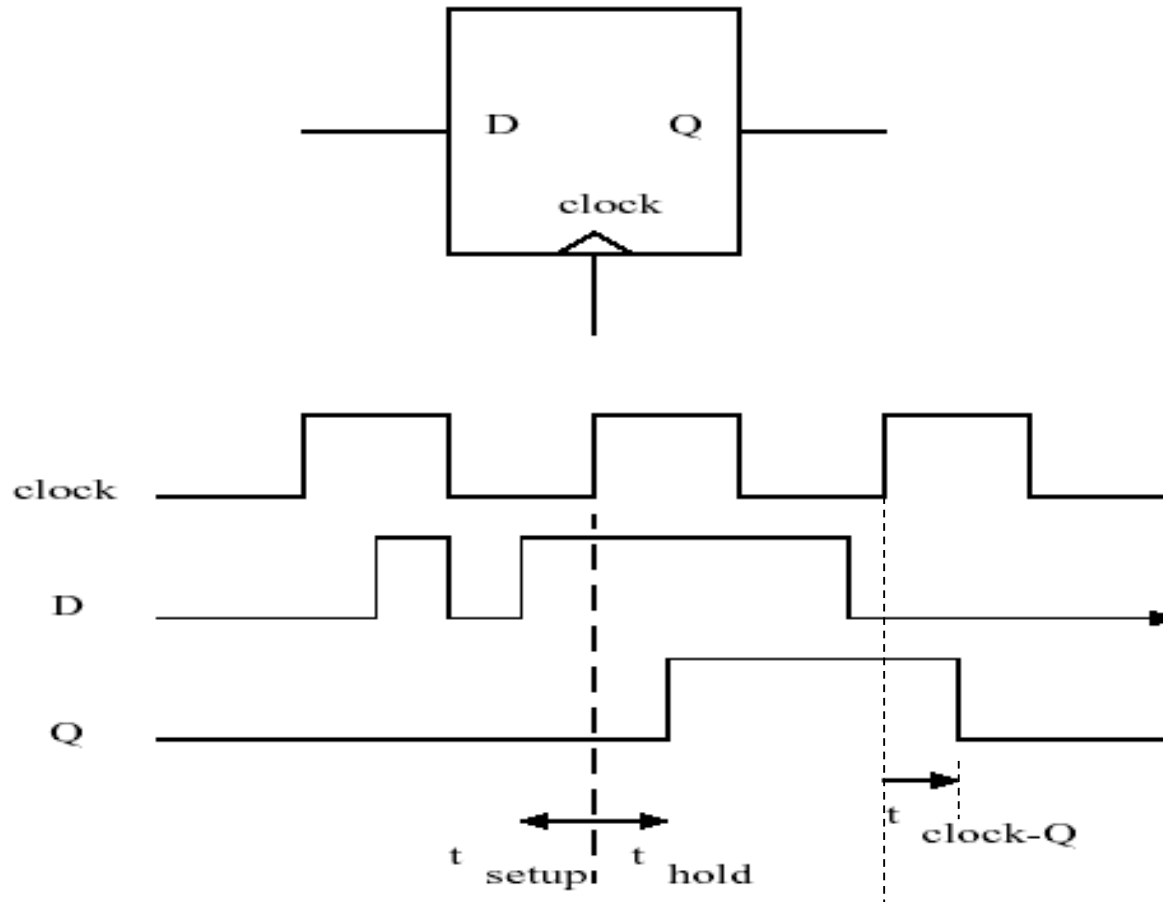

- $t_{\text{clock\_Q}}$  : D input is sampled at the rising edge of the clock and transferred to the Q output after the delay time.
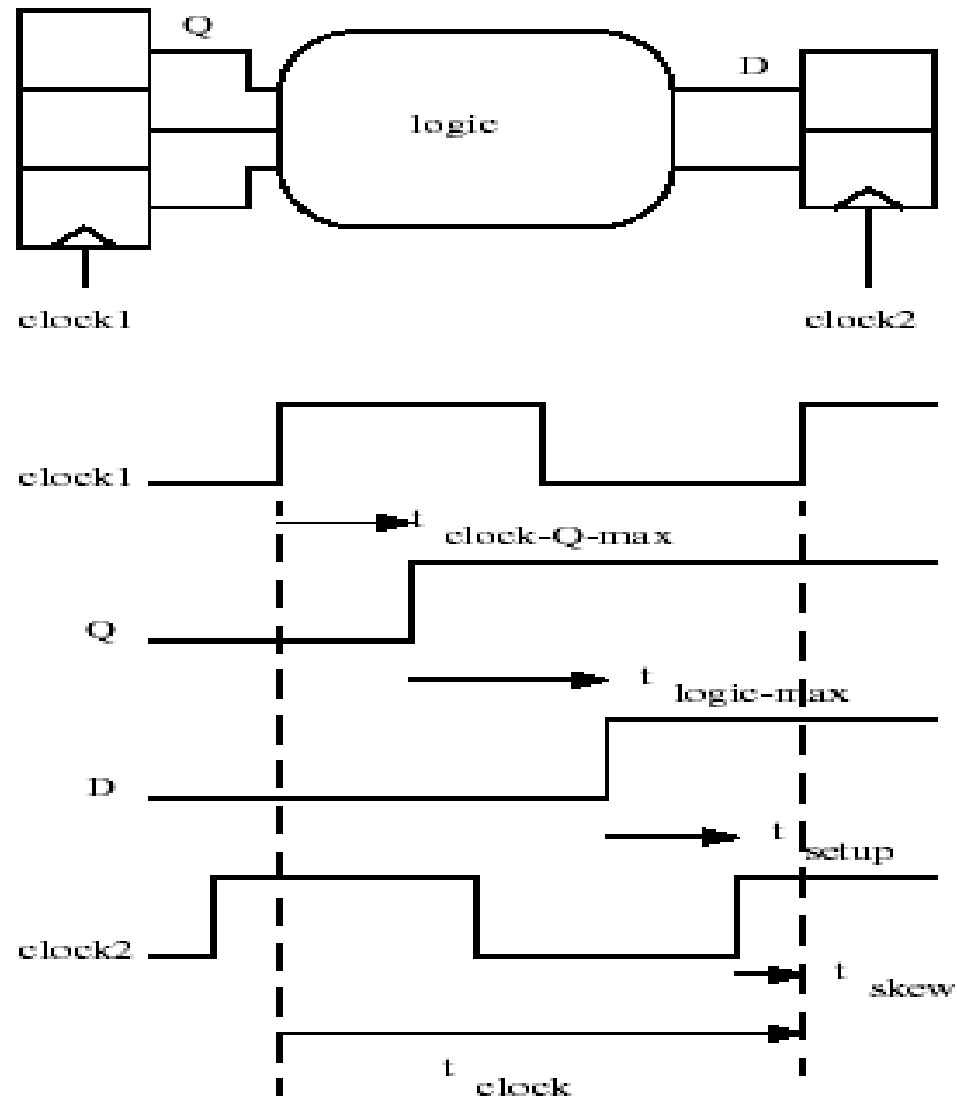
# Timing Calculations for Clock Period and Setup Violations



$$t_{clock} \geq t_{clock\_Q\_max} + \sum t_{logic\_max} + t_{setup\_max} + t_{skew}$$

where

$t_{clock\_Q\_max}$  : is the maximum delay from the clock edge on the left-side FF to the Q output changing.


$\sum t_{logic\_max}$  : is the sum of the logic delays of the gates between successive FFs.

$t_{setup\_max}$  : is the longest possible setup time requirement.

$t_{skew}$  : is the worst-case clock skew.

 
## Timing aware design - slow linear search:

```
reg [15:0] A, B, C, D, Largest;  
  
always@(A or B or C or D)  
begin  
    if (A>B) Largest = A;  
    else Largest = B;  
    if (C > Largest) Largest = C;  
    if (D > Largest) Largest = D;  
end
```


 
## Fast binary search structure

```
reg [15:0] A, B, C, D;  
wire [15:0] Large1, Large2, Largest;  
  
assign Large1 = (A>B) ? A : B;  
assign Large2 = (C>D) ? C : D;  
assign Largest = (Large1 > Large2) ? Large1 : Large2;
```




# Low Power Issues in Design

- Power Consumption in CMOS Circuits

$$i_{supply} = C_L \cdot \frac{dV}{dt}$$

$V$  : the instantaneous voltage across the capacitance.

 Circuit model for power dissipated in a CMOS gate.



$$P = i_{supply} V_{dd} = V_{dd} \cdot C_L \cdot \frac{dV}{dt}$$

$$E = \int_0^T P(t) dt = 2 \int_0^{V_{dd}} C_L dV = C_L \cdot V_{dd}^2$$

$$Power = \sum_{nodes} N_{node} \cdot C_L V_{dd}^2 \cdot f_{clock}$$

$N_{node}$  : the fraction of clock cycle; switching activity in each node.


$f_{clock}$  : the clock frequency

## Potentially power-inefficient multiplier design.

```
reg [31:0] C;  
reg [15:0] A,B;  
  
always@(posedge clock)  
    C = A * B;
```

- Let's assume that the output of multiplier is only actually used 10% clock cycle, When A or B change, the multiplier calculates a new result  $A * B$

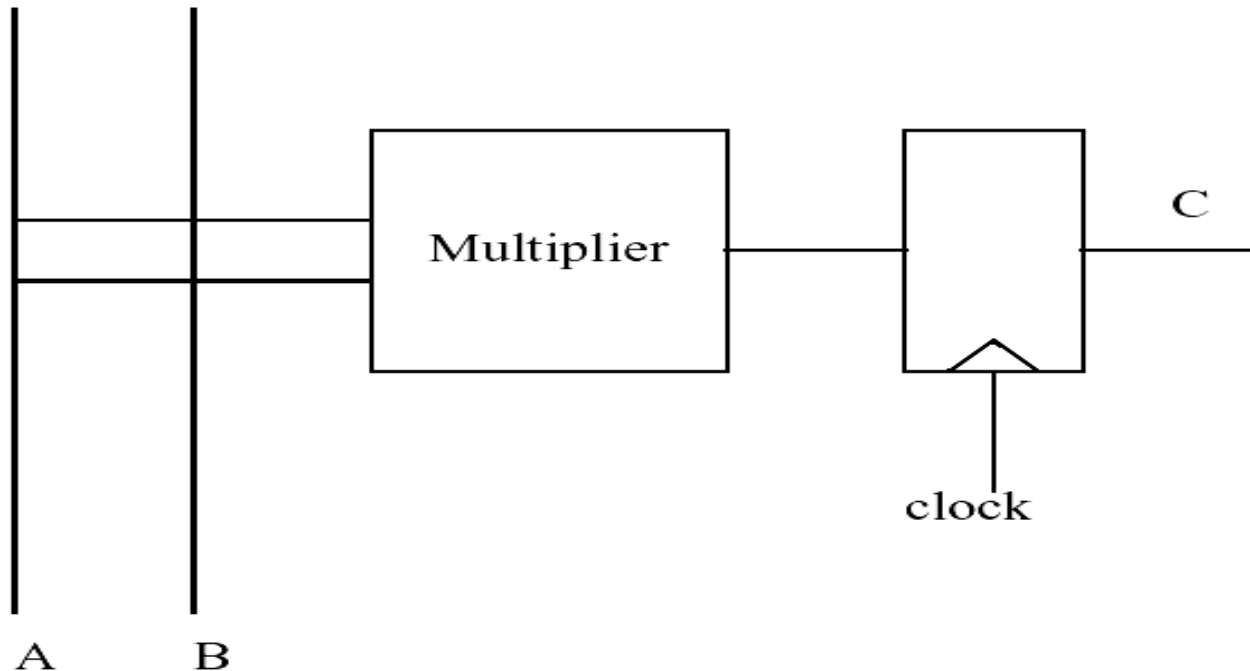⇒ For 90% cycle time, the calculation is not used and the power consumption is wasted!




## More power-efficient multiplier designs:

```
reg [31:0] C;  
reg [15:0] A,B;  
wire [15:0] Ain, Bin;  
assign Ain = GoForthAndMultiply ? A : 16'h0;  
assign Bin = GoForthAndMultiply ? B : 16'h0;  
always@(posedge clock)  
    C = Ain * Bin;
```

- The input signal change only when needed.
- Tri-state z units could be used, but makes production debug and test difficult.

=> Then, replace by 0 states.

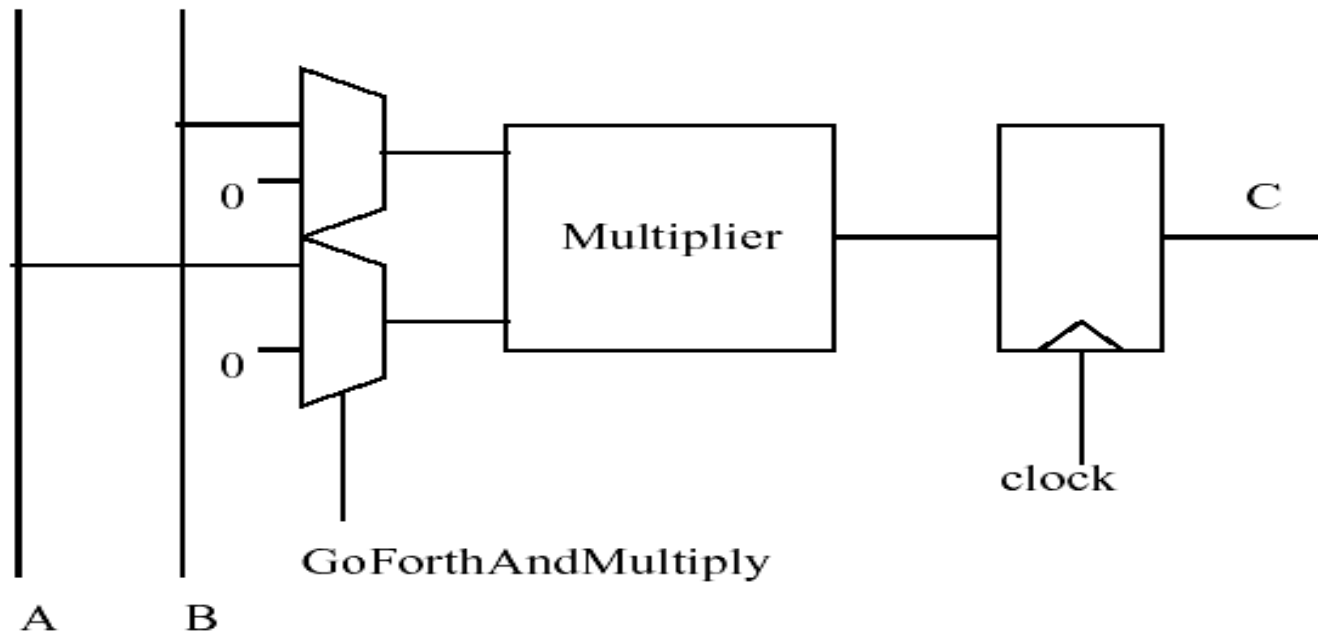



## More power-efficient multiplier designs:

```
reg [31:0] C;  
reg [15:0] A,B;  
wire [15:0] Ain, Bin;  
always@(posedge clock)  
begin  
    C <= Ain * Bin;  
    If (GoForthAndMultiply == 1)  
        begin Ain <= A; Bin <= B; end  
end
```

- **CAD tools in Low-power design**

There is now a variety of power design tools from CAD vendors .

➡ Transistor and switch level

➡ Gate level

➡ Architectural and RTL level

# Area Issues in Design

## Area-aware design: multiplier:

```
wire [15:0] A,B,C;  
wire [7:0] In1, In2, In3;  
wire      MultSelect;  
  
assign A = In1 * In2;  
assign B = In1 * In3;  
assign C = MultSelect ? A : B;
```

- Two multipliers are built, and only one of the multipliers is being used at a time.

```
wire [15:0] C;  
wire [7:0] In1, In2, In3, InSelect;  
wire      MultSelect;  
  
assign InSelect = MultSelect ? In2 : In3;  
assign C = In1 * InSelect;
```


- Only one multiplier is built.

## Area-aware design: register file:

```
module RegFile (clock, WE, WriteAddress, ReadAddress, WriteBus, ReadBus);  
  
  input clock, WE;  
  input [4:0] WriteAddress, ReadAddress;  
  input [15:0] WriteBus;  
  output [15:0] ReadBus;  
  
  reg [15:0] RegisterFile [0:31]; // thirty-two 16-bit registers  
  
  assign ReadBus = RegisterFile [ReadAddress];  
  
  always@(posedge clock)  
    if (WE) RegisterFile [WriteAddress] <= WriteBus;  
  
endmodule
```

**WE 與 WriteAddress  
無關**

 - In the above HDL codes, the synthesis tools are not very good at implementing the implies address decoders.



Modify the above HDL codes, then

```
module RegFile (clock, WE, WriteAddress, ReadAddress, WriteBus, ReadBus);  
  input clock, WE;  
  input [4:0] WriteAddress, ReadAddress;  
  input [15:0] WriteBus;  
  output [15:0] ReadBus;  
  reg [15:0] RegisterFile [0:31]; // thirty-two 16-bit registers  
  // provide one Write Enable line per register  
  wire [0:31] WElines;  
  integer i;  
  // explicitly build individual Write Enable lines by shifting WE to correct line  
  assign WElines = (WE << WriteAddress);  
  assign ReadBus = RegisterFile [ReadAddress];  
  
  always@(posedge clock)  
    for (i=0; i<=32; i=i+1)  
      if (WEline[i]) RegisterFile [i] <= WriteBus;  
endmodule
```


**WE 與 WriteAddress  
有關**

- In the above HDL codes, the design is with explicit address decode logic ( as captured in the signals “WElines” ).
- When synthesized, this design is 20% smaller and 4% faster than the simpler, implicit design ( with cell-based design).


# Some Usual Suspects
 
## Setup Violation

```
always @(posedge clk)
begin
    FFA <= D;
    FFB <= expr(FFA);
end
```



FFA propagation

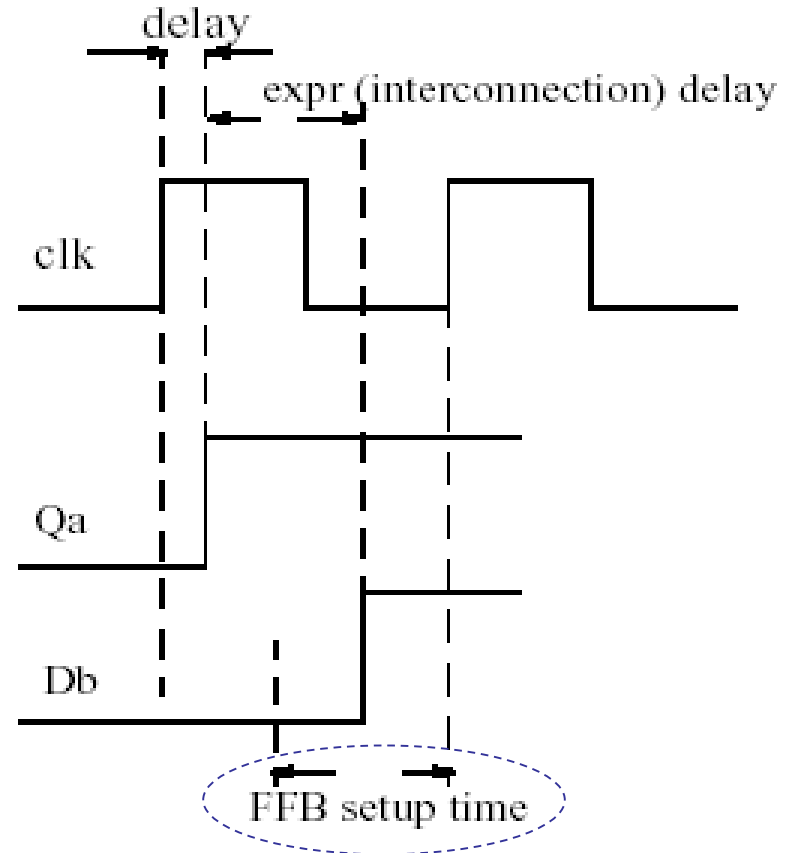



<Ref> Verilog Styles for Synthesis of Digital Systems, Smith/Franzon, Prentice-Hall 2000

pp 245 ~ 246

# Some Usual Suspects
  
## Hold Violation

```
always @(posedge clk)
begin
    RAM.select <= 1;
    expr(P.incr) <= 1;
end
```



<Ref> Verilog Styles for Synthesis of Digital Systems, Smith/Franzon, Prentice-Hall 2000

pp 245 ~ 246